

No announcements today

---

Recall:


Kirchoff's laws for electrical circuits

Source: Postnikov lecture notes

(link on 412 course website)

Let  $G$  be a (loopless) graph, and consider edges of  $G$  to represent resistors.

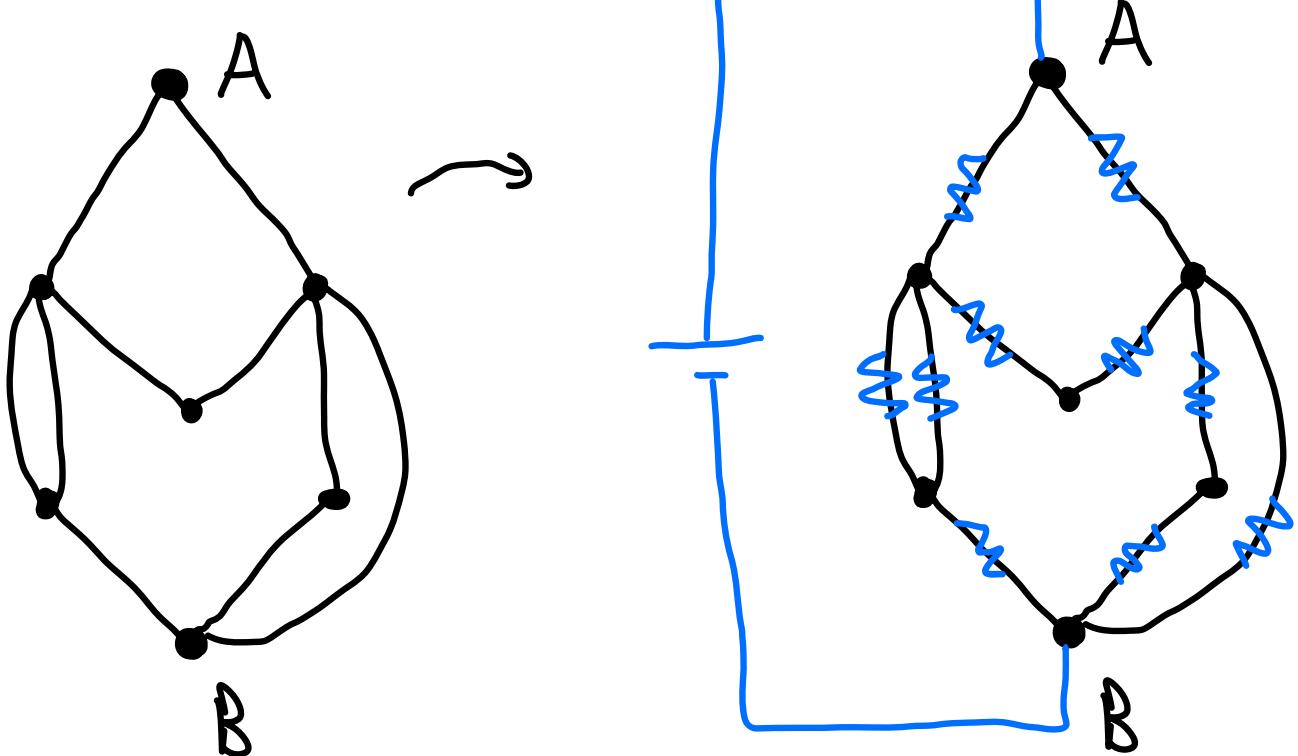Choose vertices  $A$  and  $B$  to be connected to a source of electricity



Choose any orientation  $D$  of  $G$   
 (doesn't matter which)

Quantities associated to each edge  $e$ :

- Current  $I_e$  through  $e$
- Voltage (or potential difference)  $V_e$  across  $e$
- Resistance  $R_e$  of  $e$  ( $R_e > 0$ )
- Conductance  $C_e := \frac{1}{R_e}$

Three laws:

K1: At any vertex  $v$ , the sum of the in-currents equals the sum of the out-currents:

$$\sum_{\substack{e \text{ has} \\ \text{head } v}} I_e = \sum_{\substack{e \text{ has} \\ \text{tail } v}} I_e$$

K2: For any cycle  $C$  in  $G$ , the (signed) sum of voltages is 0:

$$\sum_{e \in E(C)} \pm V_e = 0,$$

where we traverse  $C$  in either direction, and the term involving  $V_e$  is positive iff we traverse  $e$  in the way it's oriented in  $D$ .

Ohm's Law:  $\forall e \in E(D)$ ,

$$V_e = I_e R_e \quad (I_e = V_e C_e)$$

Prop:  $K_2$  is equivalent to the following condition:

$K'_2$ : There exists a (unique) function

$$U: V(G) \rightarrow \mathbb{R},$$

called the potential function, s.t.

a)  $\forall \begin{array}{c} u \\ \xrightarrow{e} \\ v \end{array}, \quad V_e = U(v) - U(u)$


b)  $U(B) = 0$

Pf: Homework!

From here on, let  $V_e = U(\text{tail}) - U(\text{head})$   
instead. Changes in blue

Goal: find the "effective resistance"  $R(G)$   
of a whole graph  $G$

Ex:

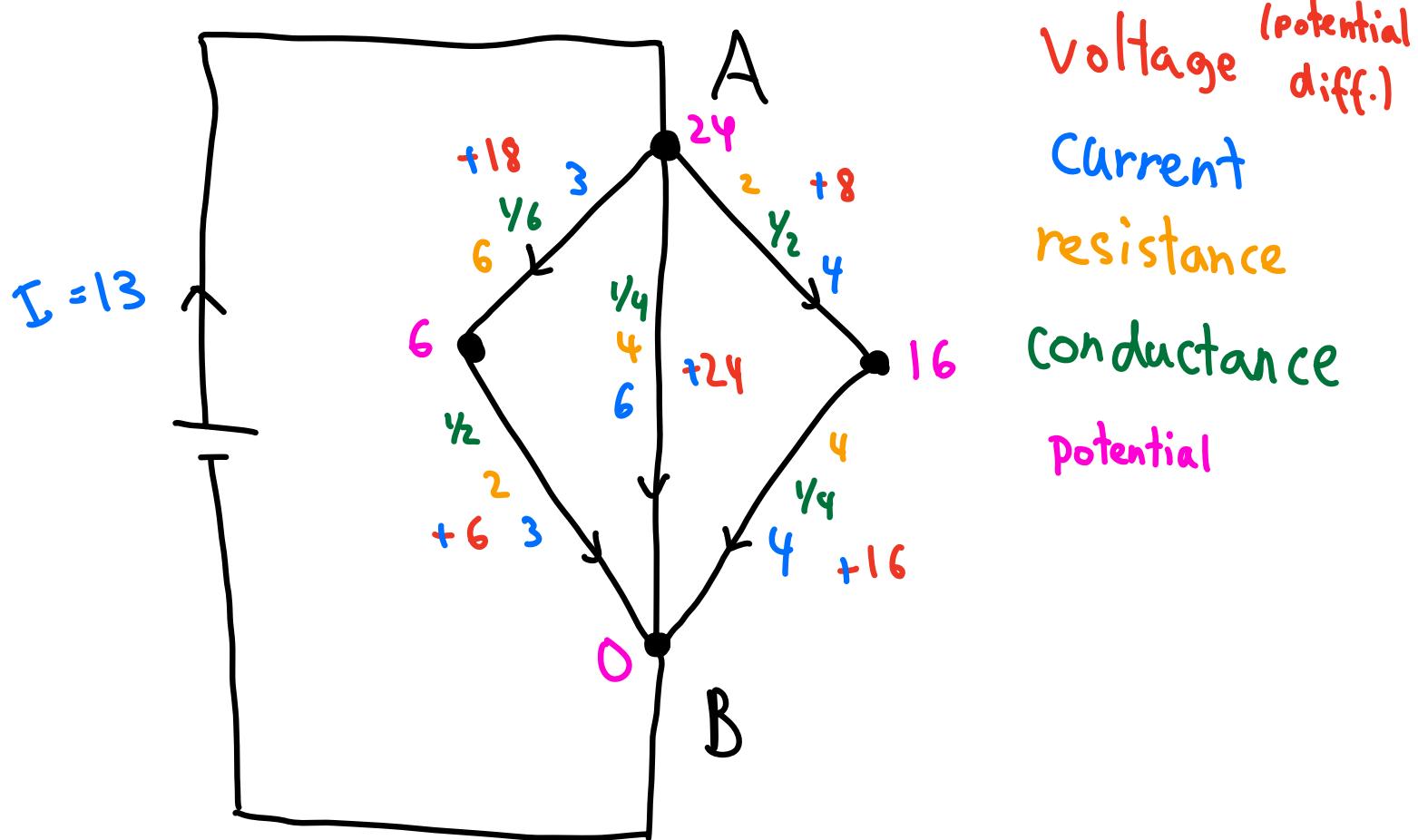

The graph  $G$  has

total potential difference  $V = 24 - 0 = 24$

$$\text{resistance } R = \frac{24}{13} \quad \left. \begin{array}{l} \\ \end{array} \right\} \text{indep. of } I$$

$$\text{conductance } C = \frac{13}{24} \quad \left. \begin{array}{l} \\ \end{array} \right\}$$

Lets combine our three laws: (v fixed)

K1:

$$\sum_{\substack{e \text{ has} \\ \text{head } v}} I_e = \sum_{\substack{e \text{ has} \\ \text{tail } v}} I_e$$

Apply Ohm's Law:

$$\sum_{\substack{e \text{ has} \\ \text{head } v}} \frac{V_e}{R_e} = \sum_{\substack{e \text{ has} \\ \text{tail } v}} \frac{V_e}{R_e}$$

$$\sum_{\substack{e \text{ has} \\ \text{head } v}} V_e C_e = \sum_{\substack{e \text{ has} \\ \text{tail } v}} V_e C_e$$

Apply K2':  $V_e = U(\text{tail}) - U(\text{head})$

$$\sum_{\substack{e \rightarrow v \\ \text{in } D}} (U(u) - U(v)) C_e = \sum_{\substack{v \rightarrow u \\ \text{in } D}} (U(v) - U(u)) C_e$$

Rearrange:

$$\sum_{\substack{u \xrightarrow[e]{} v \\ \text{in } G}} (V(v) - V(u)) c_e = 0$$

Actually, need to treat A, B differently:

$$\sum_{\substack{u \xrightarrow[e]{} v \\ \text{in } G}} (V(v) - V(u)) c_e = \begin{cases} +I, & \text{if } v = A \\ -I, & \text{if } v = B \\ 0, & \text{otherwise} \end{cases}$$

Rearrange some more

$$V(v) \left( \sum_{\substack{e \\ \text{in } G}} c_e \right) - \sum_u V(u) \left( \sum_{\substack{u \xrightarrow[e]{} v \\ \text{in } G}} c_e \right) = \begin{cases} +I, & A \\ -I, & B \\ 0, & \text{else} \end{cases}$$

Surprise — this is matrix multiplication

Order  $V(G)$  as  $v_1 = A, v_2, \dots, v_n = B$

Let  $\vec{u} = \begin{bmatrix} u(v_1) \\ \vdots \\ u(v_n) \end{bmatrix}$        $\vec{i} = \begin{bmatrix} +I \\ 0 \\ \ddots \\ 0 \\ -I \end{bmatrix}$

Then  $K\vec{u} = \vec{i}$ , where

$$k_{ij} = \begin{cases} \frac{\sum c_e}{v_i}, & \text{if } i=j \\ -\frac{\sum c_e}{v_j}, & \text{if } i \neq j \end{cases}$$

in  $G$

$K = L(G)$ , the (weighted) Laplacian matrix of  $G$ !

The weight  $\text{wt}(e) = C_e$ , the conductance of  $e$

How do we find the effective resistance  $R$ ?

Use Ohm's Law:

$$R = \frac{V}{I} = \frac{U_1 - U_n}{I} \quad V_i := U(v_i)$$

Shifting & scaling, take  $U_n = 0$ ,  $I = 1$ , so

$$R = U_1 = \begin{matrix} \text{first} \\ \text{entry} \\ \text{of} \end{matrix} L(G)^{-1} \begin{bmatrix} +1 \\ 0 \\ \vdots \\ 0 \\ -1 \end{bmatrix}$$

$$= \begin{matrix} \text{first} \\ \text{entry} \\ \text{of} \end{matrix} L^n(G)^{-1} \begin{bmatrix} -1 \\ 0 \\ \vdots \\ 0 \end{bmatrix}$$

By Cramer's Rule (applied to this situation):

$$V_n = \frac{\det L^{1,n}(G)}{\det L^n(G)}$$

By the Matrix Tree Theorem:

$$\det L^n(G) = \tau(G)$$

$$\det L^{1,n}(G) = \det L^n(\tilde{G}) = \tau(\tilde{G})$$

where  $\tilde{G} = (G \sqcup AB) \cdot AB$


(glue A and B together)

We have proven the following:


Theorem (Kirchoff):

$$R(G) = \frac{\tau(\tilde{G})}{\tau(G)}$$


**Ex:**

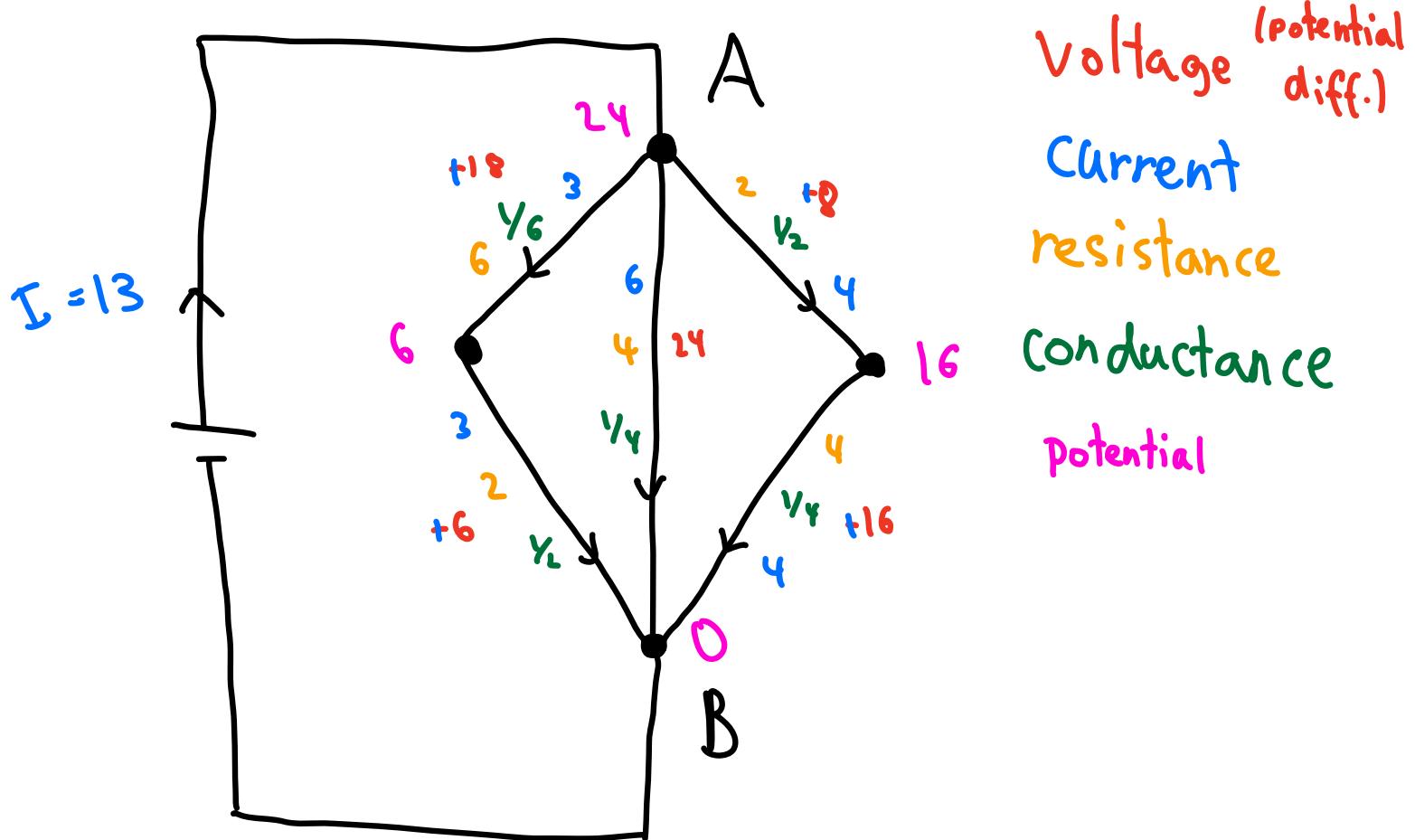


G:

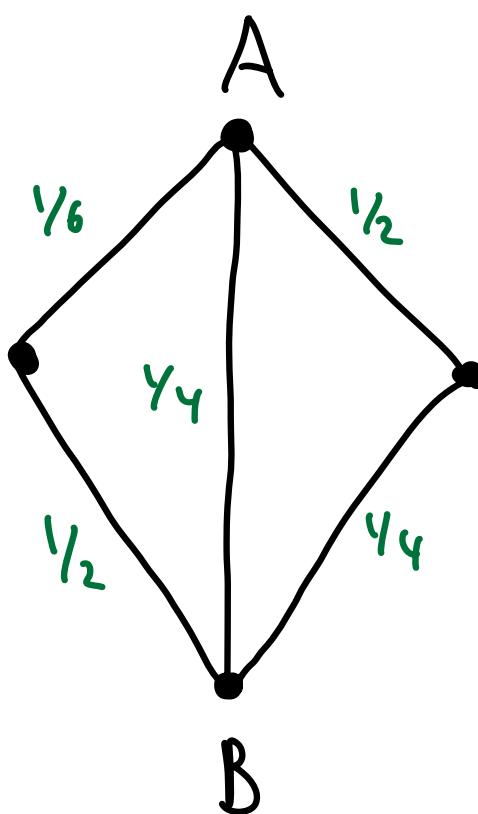


~G:

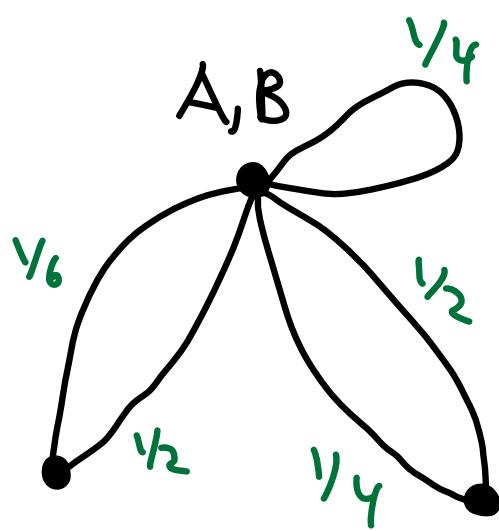


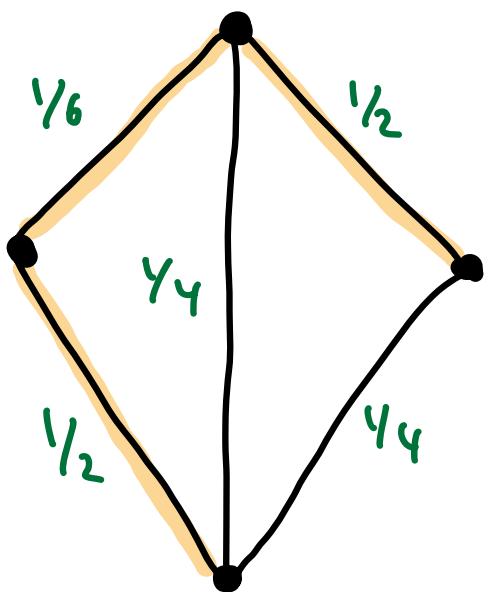


$$\frac{1}{24}$$

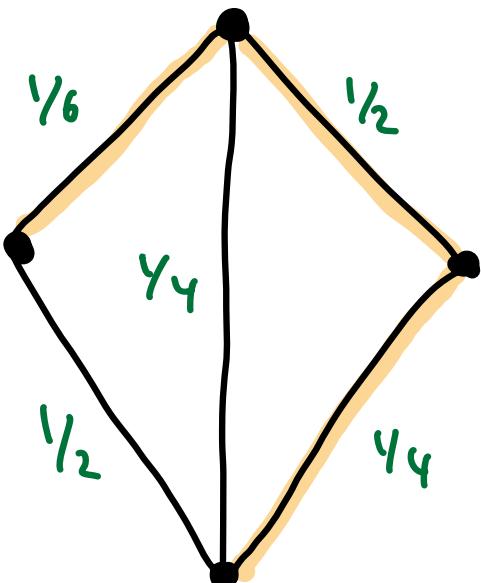


$$\frac{1}{48}$$

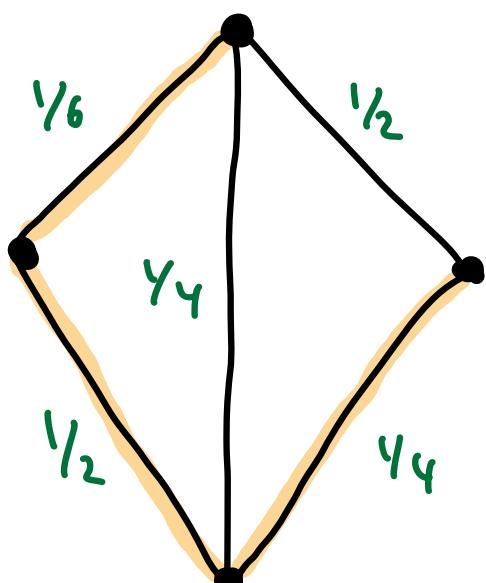


$$\frac{1}{48}$$

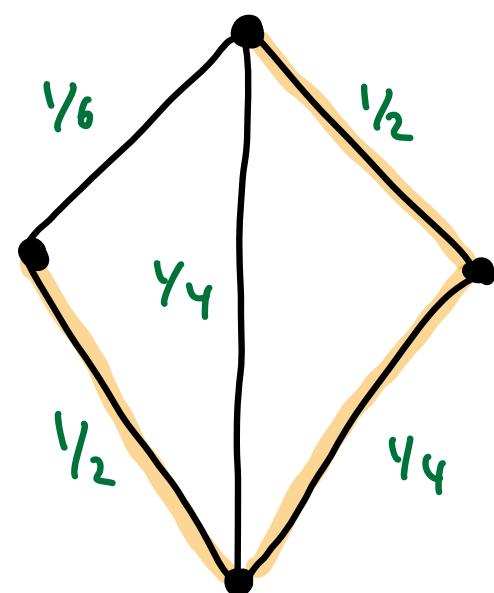


$$\frac{1}{16}$$

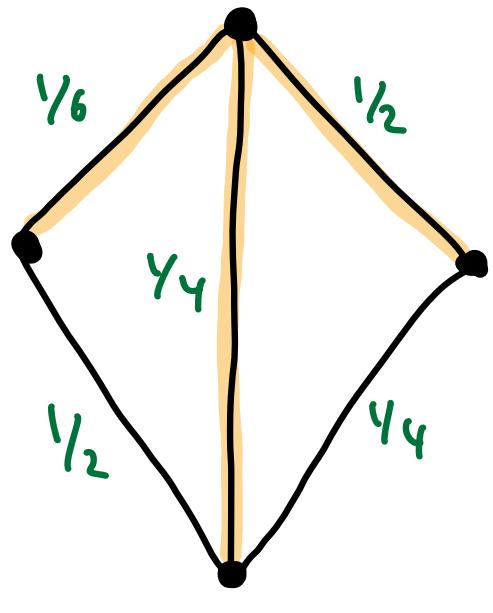


$$\frac{1}{48}$$

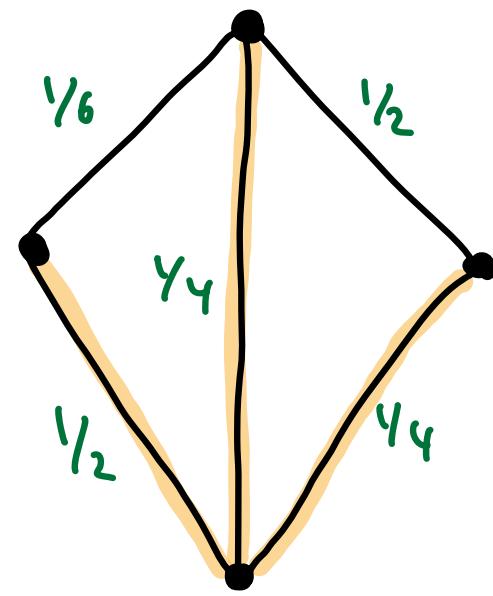

$$\frac{1}{32}$$

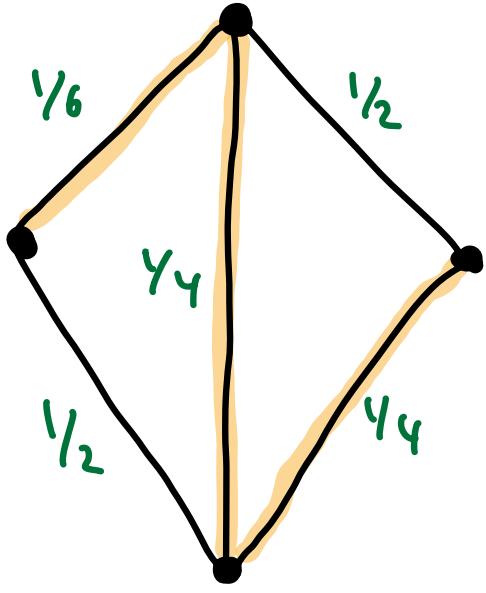


$$\frac{1}{96}$$

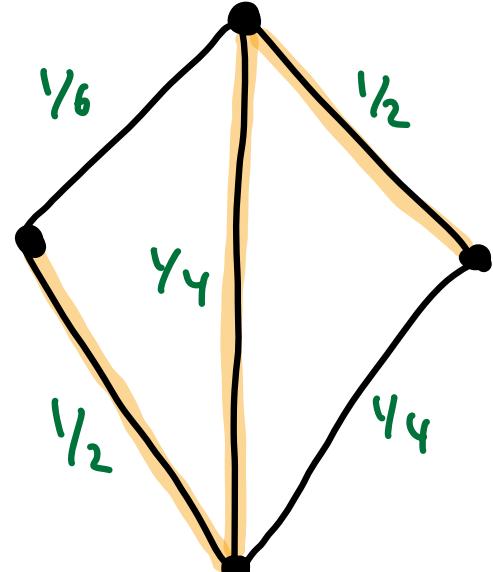


$$\frac{1}{16}$$


$$\tau(G) = \frac{13}{48}$$

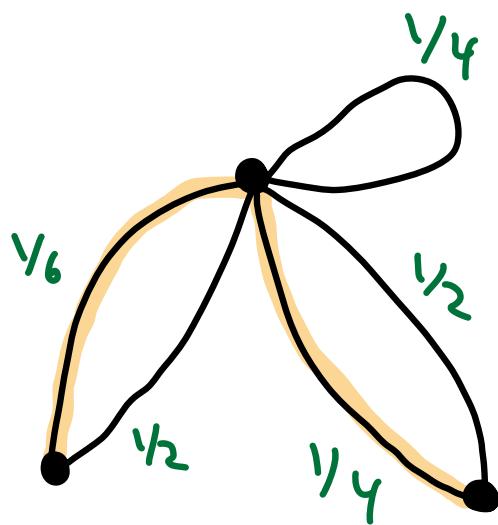


$$\frac{1}{24}$$

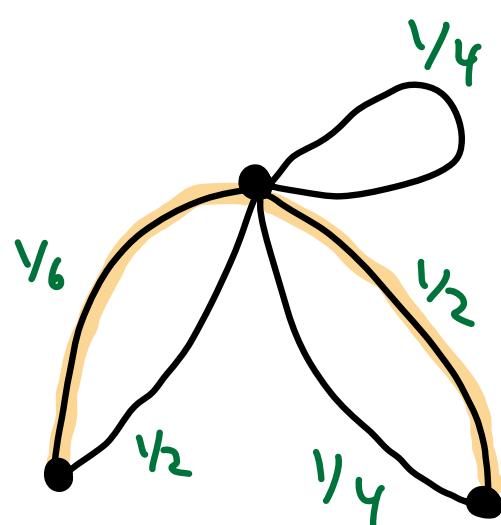

$$\frac{1}{12}$$

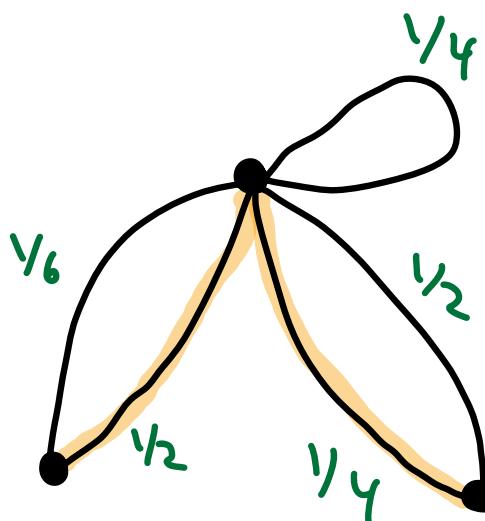

$$\frac{1}{8}$$

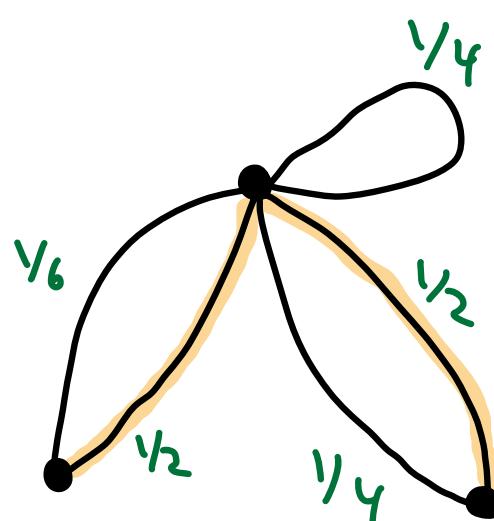

$$\frac{1}{4}$$

$$\tau(\tilde{G}) = \frac{1}{2}$$

$$R(G) = \frac{\tau(\tilde{G})}{\tau(G)} = \frac{24}{13} \quad \checkmark$$